

Design Idea DI-39

TOPSwitch-GX[®] 13 W, Universal Input DVD Supply with 70 mW No-load



Application	Device	Power Output	Input Voltage	Output Voltage	Topology
DVD	TOP244P	13 W (17 W pk)	85-265 VAC	3.3 V / 5 V / 12 V / -12 V	Flyback

Design Highlights

- High efficiency multi-output flyback (77% minimum)
- Topology scalable to higher powers
- Excellent cross-regulation
- Excellent input no-load consumption <70 mW input
- 132 kHz switching frequency allows smaller transformer
- Frequency jitter eliminates common-mode EMI choke
- >10 dB margin against CISPR22-B conducted EMI with artificial hand grounding

Operation

The TOPSwitch-GX uses current mode feedback to achieve excellent no-load standby. Components C16, R1 and Q2 provide a constant current powering the TOPSwitch-GX CONTROL pin. Resistor R2 feeds the remainder of Q2 current to the M pin, reducing TOPSwitch-GX current limit with increased current.

Resistor R11 sets the maximum current limit of the device. Components R6, Q1 and C13 implement slope compensation.

The supply operates at full frequency at high and medium power and reduces frequency at light loads. Components D9 and C10 rectify and filter the bias voltage.

TOPSwitch-GX frequency jitter allows conducted EMI compliance without a common-mode choke, using only capacitors C1, C4 and inductor L1 as an EMI filter.

Components D5 and C2 form a capacitor clamp circuit absorbing leakage inductance energy during normal operation. Zener VR1 clamps the voltage to a safe level during abnormal and transient conditions. After clamping, reverse current flows through D5, recovering some of the energy. Resistor R5 limits the reverse current and, with R7, improves EMI by limiting the ringing on the drain. Continuous mode operation allows reduced primary and secondary peak currents, optimizing cross regulation and load regulation by minimizing leakage inductance induced voltage shifts.

Resistors R15 and R16 share the feedback from the 3.3 V and 5 V outputs for good cross-regulation.

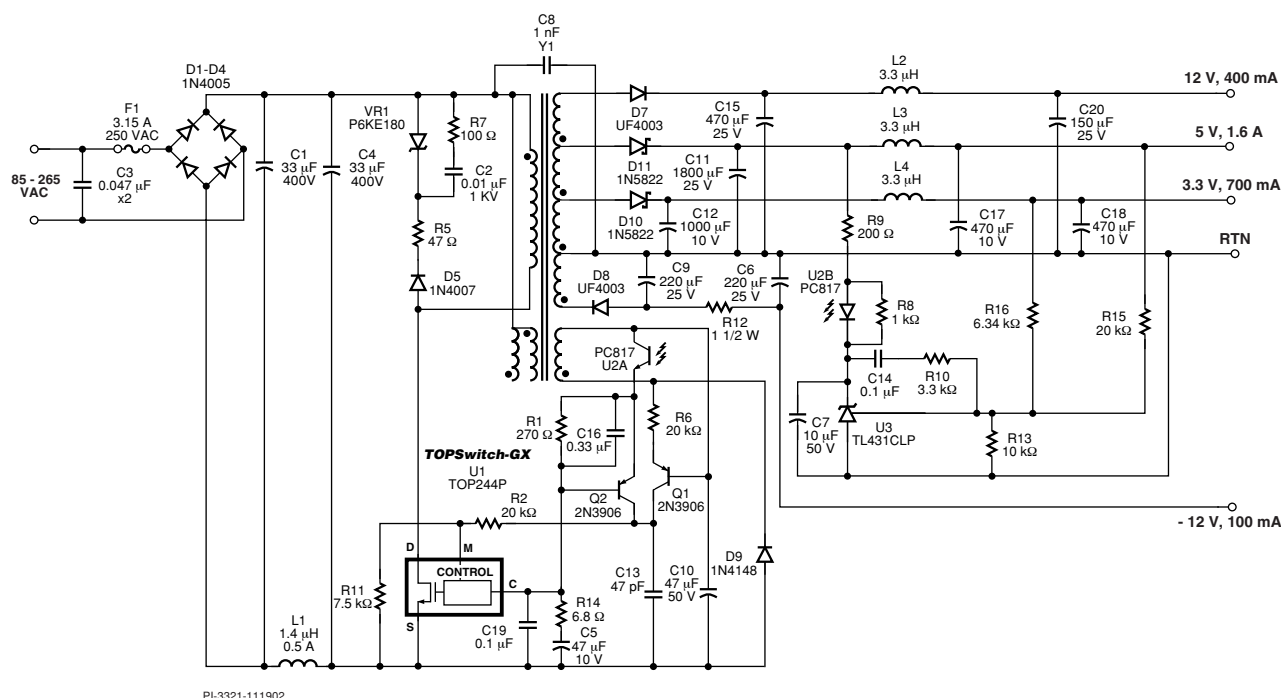


Figure 1. TOPSwitch-GX DVD Player Schematic.

Key Design Points

- Use of foil for the 3.3 V and 5 V windings also helps to optimize cross-regulation.
- Optional capacitor C7 is the “soft-finish” capacitor and prevents overshoot on startup.
- Compact layout for components D7, D10, D11, C11, C12, C15 will improve cross-regulation and efficiency. Compact layout for L2, L3, L4, C17, C18, and C20 will achieve best output ripple.
- Figure 2 shows conducted EMI at 230 VAC full load, with output “Artificial Hand” grounding. Floating output return gives lower results.
- Table 2 shows the cross regulation of the supply over load for both 115 VAC and 230 VAC.

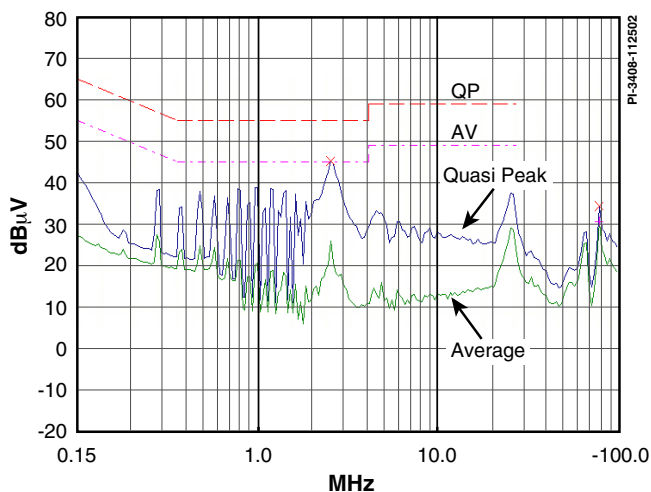


Figure 2. EMI at 230 VAC Full Load with "Artificial Hand" Grounding of Output.

TRANSFORMER PARAMETERS	
Core Material	EEL25 Himag MZ4 EEL25.4, Taiwan AL of 344 nH/T2
Bobbin	EEL25 Vertical 14 Pins
Winding Details	Shield: 32T x 2 x 32 AWG Primary: 64T x 2 x 32 AWG Bias: 10T x 4 x 32 AWG Shield: 2T x 8 x 32 AWG +3.3V: 4T x foil 0.052 x 14 mm +5V: 1T x foil 0.052 x 14 mm +12V: 4T x 4 x 32 AWG -12V: 7T x 4 x 32 AWG
Winding Order (Pin Numbers)	Shield (NC-5), tape, Primary (1-4), tape, Bias (7-6), tape, Shield (5-NC), tape, +12 V (13-8), +3.3 V (11,12-9,10), +5 V (9-10,13), tape, -12 V (14-11, 12), tape
Primary Inductance (Pins 1-4 all others open)	1.42 mH $\pm 10\%$ at 132 kHz
Primary Resonant Frequency	300 kHz minimum
Leakage Inductance	30 μ H maximum

Table 1. Transformer Construction Information.

Output Voltage (V)	Load Range (%)	Cross Regulation (%)								
		-4	-3	-2	-1	0	1	2	3	4
3.3	10-100									
5	10-100									
12	10-100									
-12	100									

Table 2. Worst Case Cross Regulation at 115 VAC and 230 VAC.

For the latest updates, visit our Web site: www.powerint.com

Power Integrations reserves the right to make changes to its products at any time to improve reliability or manufacturability. Power Integrations does not assume any liability arising from the use of any device or circuit described herein, nor does it convey any license under its patent rights or the rights of others. The products and applications illustrated herein (including circuits external to the products and transformer construction) may be covered by one or more U.S. and foreign patents or potentially by pending U.S. and foreign patent applications assigned to Power Integrations. A complete list of Power Integrations' patents may be found at www.powerint.com.

The PI Logo, **TOPSwitch**, **TinySwitch**, **LinkSwitch** and **EcoSmart** are registered trademarks of Power Integrations, Inc. **PI Expert** is a trademark of Power Integrations, Inc. ©Copyright 2002, Power Integrations, Inc.

WORLD HEADQUARTERS AMERICAS

Power Integrations, Inc.
San Jose, CA 95138 USA
Customer Service:
Phone: +1 408-414-9665
Fax: +1 408-414-9765
e-mail: usasales@powerint.com

CHINA

Power Integrations International Holdings, Inc.
China
Phone: +86-755-8367-5143
Fax: +86-755-8377-9610
e-mail: chinasales@powerint.com

EUROPE & AFRICA

Power Integrations (Europe) Ltd.
United Kingdom
Phone: +44-1344-462-300
Fax: +44-1344-311-732
e-mail: eurosales@powerint.com

KOREA

Power Integrations
International Holdings, Inc.
Seoul, Korea
Phone: +82-2-782-2840
Fax: +82-2-782-4427
e-mail: koreasales@powerint.com

SINGAPORE

Power Integrations, Singapore
Republic of Singapore 308900
Phone: +65-6358-2160
Fax: +65-6358-2015
e-mail: singaporesales@powerint.com

JAPAN

Power Integrations, K.K.
Keihin-Tatemono 1st Bldg.
Japan
Phone: +81-45-471-1021
Fax: +81-45-471-3717
e-mail: japansales@powerint.com

APPLICATIONS HOTLINE

World Wide +1-408-414-9660

TAIWAN

Power Integrations
International Holdings, Inc.
Taipei, Taiwan
Phone: +886-2-2727-1221
Fax: +886-2-2727-1223
e-mail: taiwansales@powerint.com

INDIA (Technical Support)

Innovatech
Bangalore, India
Phone: +91-80-226-6023
Fax: +91-80-228-9727
e-mail: indiasales@powerint.com

APPLICATIONS FAX

World Wide +1-408-414-9760