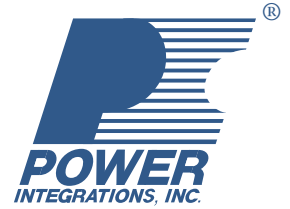


Design Idea DI-53

DPA-Switch™

50 W DC-DC Dual Output Converter



Application	Device	Power Output	Input Voltage	Output Voltage	Topology
Telecom	DPA425R	50 W	36-75 VDC	5 V & 3.3 V	Forward Sync. Rect.

Design Highlights

- High efficiency: 90% at 36 VDC using synchronous rectification
- Dual output with tight cross-regulation $\pm 4\%$ from zero to full load on both outputs
- Output overload, open loop and thermal protection
- 300 kHz switching frequency to allow sufficient transformer reset time with sync rectification
- 3.85 x 2.25 x 0.6 inch (~ 9.62 W/in³)

Operation

DPA-Switch greatly simplifies the design compared to a discrete implementation. This design uses a coupled output inductor and synchronous rectification to achieve excellent cross-regulation and high efficiency.

Resistor R1 programs the under/over voltages and linearly reduces the maximum duty cycle with input voltage to prevent core saturation during load transients. Components D1, D2, C9 and L2 implement a resonant clamp circuit to catch and

recirculate the transformer leakage energy during normal operation, with Zener VR1 providing absolute clamping for transient conditions.

Capacitor C21 charges the gate of Q2, the forward synchronous rectifier MOSFET of the 5 V output. Resistor R21 limits gate oscillation and R22 provides gate pull-down. Zener diode VR20 limits the Q2 gate voltage during conduction and also reverse charges C21 during the Q2 off time. The same drive technique is used for the forward synchronous rectifier MOSFET (Q4) of the 3.3 V output (with C22, R24, R25, and VR21).

MOSFETs Q1 and Q3 are driven via resistors R23 and R26 from the transformer (T1) reset voltage and operate only when Q2 and Q4 are off. Diodes D20 and D21 provide a conduction path for the output inductor (L4) current when the transformer reset is complete.

A winding on the coupled inductor L4, along with diode D4 and capacitor C9, provide the DPA-Switch bias voltage.

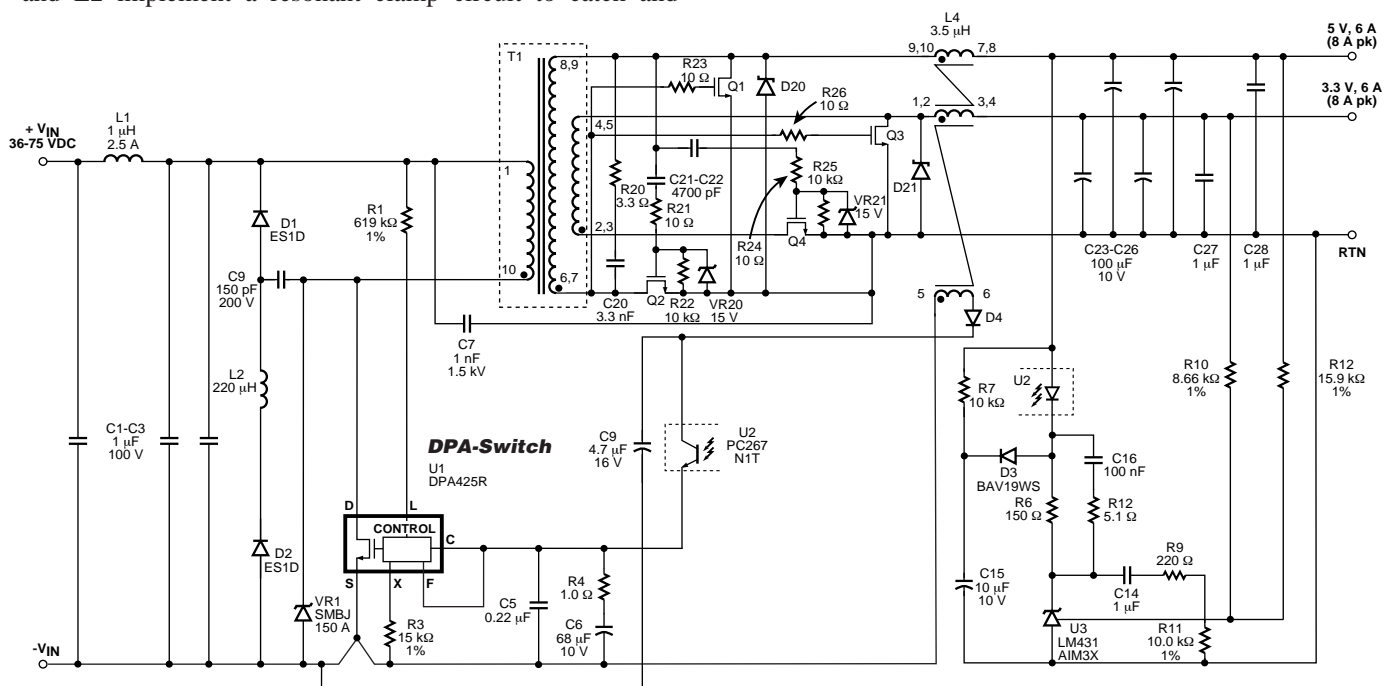


Figure 1. DPA425R - 50 W, 5 V, 6 A and 3.3 V, 6 A DC-DC Converter.

Key Design Points

- Capacitors C_{20} , C_{Q1gs} and C_{Q3gs} will all load transformer reset. Choose values to ensure sufficient reset at low line and safe maximum drain voltage at high line. Also use 300 kHz operation for longest reset time.
- Capacitors C_{21} and C_{22} will capacitively drive MOSFET gate capacitances C_{Q2gs} and C_{Q4gs} (respectively). C_{21} and C_{22} should be chosen to ensure that gate drive voltage attains turn-on threshold of MOSFET ($V_{g_{TH}}$), at worst case conditions (low line for forward MOSFET).
- Reduce transformer leakage inductance by filling each winding layer across the entire width of the bobbin.
- Higher efficiency (+1%) can be achieved by using a DPA426R and increasing R3 to reduce the internal current limit.

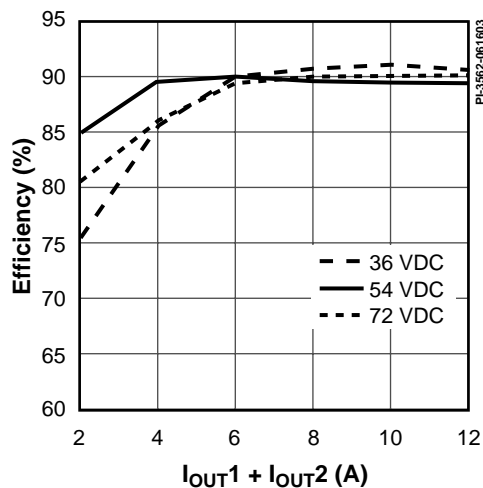


Figure 2. Efficiency vs. Output Power.

TRANSFORMER PARAMETERS	
Core Material	Ferroxcube P/N: EFD25-3F3, ungapped
Bobbin	10-pin EFD25 surface mount bobbin
Winding Details	Primary 11T, 4 x 28 AWG 3.3 V 2T, 2 x 4 x 26 AWG 5 V 3T, 2 x 4 x 26 AWG
Winding Order and Pin Numbers	5 V (6, 7-8, 9), Primary (1-10), 3.3 V (4.5-2.3)
Primary Inductance	250 μ H \pm 25% at 300 kHz
Primary Resonant Frequency	3.8 MHz (minimum)
Leakage Inductance	0.8 μ H (maximum)

Table 1. Transformer Design Parameters.

INDUCTOR PARAMETERS	
Core Material	Ferroxcube P/N: EFD25-3F3 ungapped
Bobbin	10-pin EFD20 surface mount bobbin
Winding Details	5 V 6T, 2 x 4 x 26 AWG 3.3 V 4T, 2 x 4 x 26 AWG Bias 12T, 1 x 30 TIW
Winding Order and Pin Numbers	5 V (9, 10-7, 8), 3.3 V (1, 2-3, 4), Bias (FL1-FL2)
Inductance	Pin (1, 2-3, 4): 3.5 μ H \pm 10% at 300 kHz

Table 1. Inductor Design Parameters.

For the latest updates, visit our Web site: www.powerint.com

Power Integrations reserves the right to make changes to its products at any time to improve reliability or manufacturability. Power Integrations does not assume any liability arising from the use of any device or circuit described herein, nor does it convey any license under its patent rights or the rights of others. The products and applications illustrated herein (including circuits external to the products and transformer construction) may be covered by one or more U.S. and foreign patents or potentially by pending U.S. and foreign patent applications assigned to Power Integrations. A complete list of Power Integrations' patents may be found at www.powerint.com.

The PI Logo, TOPSwitch, TinySwitch, LinkSwitch and EcoSmart are registered trademarks of Power Integrations, Inc. PI Expert and DPA-Switch are trademarks of Power Integrations, Inc. ©Copyright 2003, Power Integrations, Inc.

WORLD HEADQUARTERS

Power Integrations, Inc.
San Jose, CA, USA
Phone: +1 408-414-9200

AMERICAS

Power Integrations, Inc.
Buford, GA, USA
Phone: +1 678-714-6033

CHINA (SHANGHAI)

Power Integrations Intl. Holdings, Inc.
Shanghai, China
Phone: +86-21-6215-5548

CHINA (SHENZHEN)

Power Integrations Intl. Holdings, Inc.
Shenzhen, China
Phone: +86-755-8367-5143

GERMANY

Power Integrations GmbH
Munich, Germany
Phone: +49-895-527-3910

INDIA (TECHNICAL SUPPORT)

Innovatech
Bangalore, India
Phone: +91-80-226-6023

ITALY

Power Integrations S.r.l.
Milano, Italy
Phone: +39-028-928-6001

JAPAN

Power Integrations, K.K.
Kanagawa, Japan
Phone: +81-45-471-1021

KOREA

Power Integrations Intl. Holdings, Inc.
Seoul, Korea
Phone: +82-2-782-2840

SINGAPORE (ASIA PACIFIC HQ)

Power Integrations Singapore Pte. Ltd.
Singapore
Phone: +65-6358-2160

TAIWAN

Power Integrations Intl. Holdings, Inc.
Taipei, Taiwan
Phone: +886-2-2727-1221

UK (EUROPE & AFRICA HQ)

Power Integrations (Europe) Ltd.
Bracknell, Berkshire, United Kingdom
Phone: +44-1344-462-300

APPLICATIONS HOTLINE

Phone: +1 408-414-9660
Fax: +1 408-414-9760

CUSTOMER SERVICE

Phone: +1 408-414-9665
Fax: +1 408-414-9765

For a complete list of our Worldwide Sales Representatives & Distributors visit our Web site:
www.powerint.com

