

# Power Supply Considerations for Atmel® Capacitive-touch ICs

## 1. Introduction

This application note discusses the dedicated power supply arrangement for Atmel capacitive touch-sensitive integrated circuits (QT™ ICs).

## 2. Why Do I Need a Special Power Supply?

QT ICs derive their internal reference from the Vdd power supply. It is therefore important to ensure that Vdd is stable and free of electrical noise. The proprietary drift compensation algorithms of the QT IC are designed to overcome long-term drift. Nevertheless, transient spikes of  $\pm 10$  mV can cause erratic behaviour such as false key activations, stuck keys, and loss of touch detection.

A simple and inexpensive regulator circuit eliminates these potential problems.

## 3. General Recommendations

### Do:

- Use a dedicated regulator to power the QT IC.
- Place the regulator as close as possible to the QT IC.
- Use a GROUND plane under the regulator and under the Vss pins of the QT IC.
- For PCBs with a GROUND plane layer, extend the plane under communications circuits, any oscillator or crystal, and also decoupling capacitors.
- Place a 0.1  $\mu$ F decoupling capacitor in close physical proximity to each Vdd pin.

### Don't:

- Share Vdd with other logic circuitry or light-emitting diodes (LED).
- Use long power and GROUND traces between the regulator and the QT IC.
- Extend the GROUND plane beneath the sense pins of the QT IC, Cs capacitors, Rs resistors, or any sense line traces.

## 4. Low Drop-out (LDO) Regulator

QT ICs are optimized for low power operation. To conserve power, the device mostly operates in an ultra-low-power sleep mode in which minimal current ( $\mu$ A) is drawn. Periodically, the QT IC wakes up to perform sampling and communication routines that consume mA of current.

The poor load step response of some LDO regulators is well-known, often resulting in significant output transients when the load increases from  $\mu$ A to mA, causing erratic sensor operation. Care must be taken in the selection and use of LDO regulators.

[Figure 4-1](#) shows the circuit for a Seiko S-817 series LDO regulator.




## Power Supply Considerations for QT ICs

## Application Note QTAN0015



**Figure 4-1.** LDO Regulator Circuit

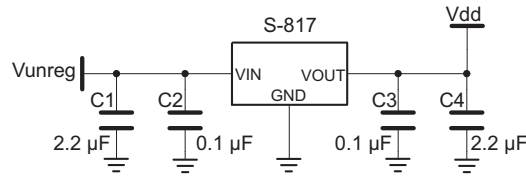


The Seiko S-817 regulator has a good load step response and reliable performance when used with QT ICs. Low quiescent current makes the S-817 regulator especially suitable for battery-driven applications.

C2 and C3 should be good quality ceramic capacitors, placed as close as possible to the regulator. An additional ceramic capacitor should be placed close to the Vdd pin on the QT IC.

## 5. Standard Linear Regulator

Figure 5-1 shows the circuit for an LM78L05 linear regulator.

**Figure 5-1.** Linear Regulator Circuit (LM78L05)

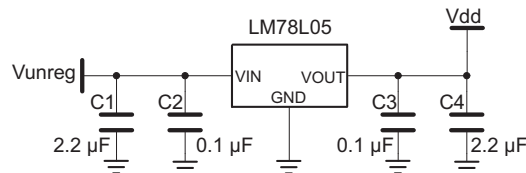

C2 and C3 should be good quality ceramic capacitors, placed as close as possible to the regulator. An additional ceramic capacitor should be placed close to the Vdd pin on the QT IC.

## 6. Direct Battery Power

The internal resistance of a battery causes the voltage to drop as the load increases, so load variations result in voltage transients. As the battery ages and discharges, its internal resistance increases and the transient effects worsen. To overcome these characteristics, QT ICs should be powered from an LDO regulator connected between the QT IC and the battery.

Exceptionally, a QT IC can be safely powered directly from the battery, but this can only be done in applications in which the battery load remains relatively constant. Particularly on older batteries, a delta value of >10 mV can be caused merely by flashing an LED or driving a small relay coil.

## 7. Associated Publications

The following document published by Atmel's Touch Technology Division is also of interest:

- QTAN0017 – Checking the Effects of External Noise on Atmel Capacitive-touch ICs

**Notes**



## Headquarters

---

**Atmel Corporation**  
2325 Orchard Parkway  
San Jose, CA 95131  
USA  
Tel: 1(408) 441-0311  
Fax: 1(408) 487-2600

## International

---

**Atmel Asia**  
Unit 01-05 & 16, 19/F  
BEA Tower, Millennium City 5  
418 Kwun Tong Road  
Kwun Tong  
Kowloon  
Hong Kong  
Tel: (852) 2245-6100  
Fax: (852) 2722-1369

**Atmel Europe**  
Le Krebs  
8, Rue Jean-Pierre Timbaud  
BP 309  
78054 Saint-Quentin-en-  
Yvelines Cedex  
France  
Tel: (33) 1-30-60-70-00  
Fax: (33) 1-30-60-71-11

**Atmel Japan**  
9F, Tonetsu Shinkawa Bldg.  
1-24-8 Shinkawa  
Chuo-ku, Tokyo 104-0033  
Japan  
Tel: (81) 3-3523-3551  
Fax: (81) 3-3523-7581

**Touch Technology Division**  
1 Mitchell Point  
Ensign Way  
Hamble  
Southampton  
Hampshire SO31 4RF  
United Kingdom  
Tel: (44) 23-8056-5600  
Fax: (44) 23-8045-3939

## Product Contact

---

**Web Site**  
[www.atmel.com](http://www.atmel.com)

**Technical Support**  
[qprox.support@atmel.com](mailto:qprox.support@atmel.com)

**Sales Contact**  
[qprox.sales@atmel.com](mailto:qprox.sales@atmel.com)

**Literature Requests**  
[www.atmel.com/literature](http://www.atmel.com/literature)

---

**Disclaimer:** The information in this document is provided in connection with Atmel products. No license, express or implied, by estoppel or otherwise, to any intellectual property right is granted by this document or in connection with the sale of Atmel products. **EXCEPT AS SET FORTH IN ATMEL'S TERMS AND CONDITIONS OF SALE LOCATED ON ATMEL'S WEB SITE, ATMEL ASSUMES NO LIABILITY WHATSOEVER AND DISCLAIMS ANY EXPRESS, IMPLIED OR STATUTORY WARRANTY RELATING TO ITS PRODUCTS INCLUDING, BUT NOT LIMITED TO, THE IMPLIED WARRANTY OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, OR NON-INFRINGEMENT. IN NO EVENT SHALL ATMEL BE LIABLE FOR ANY DIRECT, INDIRECT, CONSEQUENTIAL, PUNITIVE, SPECIAL OR INCIDENTAL DAMAGES (INCLUDING, WITHOUT LIMITATION, DAMAGES FOR LOSS AND PROFITS, BUSINESS INTERRUPTION, OR LOSS OF INFORMATION) ARISING OUT OF THE USE OR INABILITY TO USE THIS DOCUMENT, EVEN IF ATMEL HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.** Atmel makes no representations or warranties with respect to the accuracy or completeness of the contents of this document and reserves the right to make changes to specifications and product descriptions at any time without notice. Atmel does not make any commitment to update the information contained herein. Unless specifically provided otherwise, Atmel products are not approved for use in automotive applications, medical applications (including, but not limited to, life support systems and other medical equipment), avionics, nuclear applications, or other high risk applications (e.g., applications that, if they fail, can be reasonably expected to result in significant personal injury or death).

© 2008 Atmel Corporation. All rights reserved. Atmel®, Atmel logo and combinations thereof, and others are registered trademarks, QT™ and others are trademarks of Atmel Corporation or its subsidiaries. Other terms and product names may be registered trademarks or trademarks of others.