VI TELEFILTER Application Note TFS 210C - 1/2

### 1. General

The filter is single ended driven. It is matched to 50  $\Omega$ 

The matching element values given below are valid on the test PCB. If the parasitics on the customer PCB and on this PCB are different, the matching elements have to be optimised regarding the circuit and PCB design.

The matching elements have been chosen from the E12- series (European standard series with fixed tolerances).


## 2. Theoretical matching

The termination impedances of the filter are:

source impedance: 295  $\Omega$  || 1,15 pF load impedance: 295  $\Omega$  || 1,15 pF

The values of the matching elements which are given below are calculated from the source and load impedance. If the values of the matching elements are not equal to standard values the best standard values are given in brackets.


#### 50 Ω test circuit 1

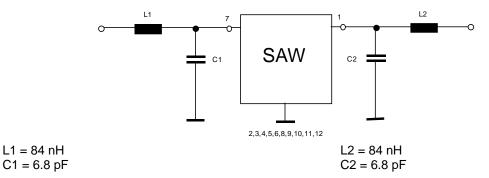

### 50 Ω test circuit 2

C1 = 6.8 pF

L1 =126 nH

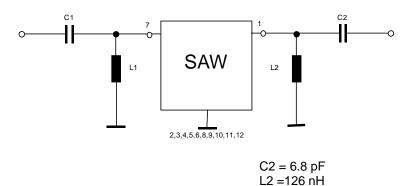


VI TELEFILTER
Potsdamer Straße 18
D 14 513 TELTOW / Germany
Tel: (+49) 3328 4784-0 / Fax: (+49) 3328 4784-30
E-Mail: tft@telefilter.com

Vectron International, Inc. 267 Lowell Road Hudson, NH 03051 / USA Tel: (603) 598-0070 Fax: (603) 598-0075 E-Mail: vti@vtinh.com VI TELEFILTER Application Note TFS 210C - 2/2
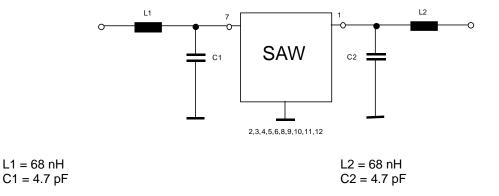
# 3. Matching on the PCB

For example: PCB with 50  $\Omega$  test circuit 1



The matching on the PCB does slightly differ from the theoretical matching. The reason for that are parasitics of the PCB.

If the parasitics on the customer board (mentioned parasitics, additional parasitics of active parts) are different to this PCB the matching elements have to be slightly adjusted.

In case of questions please contact us to

VI TELEFILTER
Potsdamer Straße 18
D 14 513 TELTOW / Germany
Tel: (+49) 3328 4784-0 / Fax: (+49) 3328 4784-30
E-Mail: tft@telefilter.com

Vectron International, Inc. 267 Lowell Road Hudson, NH 03051 / USA Tel: (603) 598-0070 Fax: (603) 598-0075 E-Mail: vti@vtinh.com