

Four-layer demonstration board based on the STA333IS

Introduction


The STEVAL-CCA053V1 is a four-layer demonstration board designed for the evaluation of the STA333IS two-channel, high-efficiency Sound Terminal[®] device.

The purpose of this application note is to show:

- how to connect the STA333IS demonstration board
- the performance of the STA333IS device
- how to avoid critical board and layout issues

All the results and characterization data included in this application note have been measured using Audio Precision equipment. Reference documents consist of the STA333IS datasheet, schematic diagrams and PCB layout.

Figure 1. STEVAL-CCA053V1

 

Contents

1	Test conditions and connections of demonstration board	4
1.1	Power supply signal and interface connection	4
1.2	Output configuration	4
1.3	Required equipment	4
1.4	Board connections	5
2	Schematic diagram and PCB layout	6
2.1	Schematic	6
2.2	PCB layout	7
2.3	Bill of material	8
3	APWorkbench settings	9
4	Test results	10
5	Thermal test - $V_{CC} = 12.5\text{ V}$, 1 kHz, load= 8 W (stereo)	14
5.1	Test conditions	14
5.2	Test results	14
6	Design guidelines for schematic and PCB layout	15
6.1	General	15
6.2	Decoupling capacitors	15
6.3	Snubber network	15
6.4	PCB layout	16
6.4.1	Snubber layout	16
6.4.2	V_{CC} traces	16
6.4.3	Ground plane and heatsink	17
6.4.4	Output filter	18
6.4.5	V_{CC} filter for high frequency	18
7	Revision history	19

List of figures

Figure 1.	STEVAL-CCA053V1	1
Figure 2.	Demonstration board (four-layer) - connectors	5
Figure 3.	Schematic diagram - part 1	6
Figure 4.	Schematic diagram - part 2 (connectors)	7
Figure 5.	STA333IS demonstration board - four-layer PCB	7
Figure 6.	APWorkbench - device selection	9
Figure 7.	APWorkbench - control panel	9
Figure 8.	THD+N vs. power - $V_{CC} = 12.5\text{ V}$, load = 8 W, 1 kHz	10
Figure 9.	THD+N vs. frequency - $V_{CC} = 12.5\text{ V}$, load = 8 W, $P_{out} = 1\text{ W}$ at 1 kHz	10
Figure 10.	Frequency response - $V_{CC} = 12.5\text{ V}$, load = 8 W, $P_{out} = 1\text{ W}$ at 1 kHz	11
Figure 11.	Crosstalk - $V_{CC} = 12.5\text{ V}$, load = 8 W, $P_{out} = 1\text{ W}$ at 1 kHz	11
Figure 12.	FFT - $V_{CC} = 12.5\text{ V}$, load = 8 W, $P_{out} = 1\text{ W}$ at 1 kHz	12
Figure 13.	Output power vs. supply voltage - load = 8 W, 1 kHz	12
Figure 14.	Efficiency - $V_{CC} = 12.5\text{ V}$, 1 kHz, load = 8 W (stereo)	13
Figure 15.	Thermal analysis - $V_{CC} = 12.5\text{ V}$ - 2 x 10 W at 1 kHz	14
Figure 16.	Snubber network	16
Figure 17.	PCB layout recommendations - star routing V_{CC} traces	16
Figure 18.	PCB layout recommendation - large ground plane on the top side	17
Figure 19.	PCB layout recommendation - large ground plane on the inner layer 2	17
Figure 20.	PCB layout recommendation - large ground plane on the inner layer 3	17
Figure 21.	PCB layout recommendation - large ground plane on the bottom side	17
Figure 22.	Output filter	18
Figure 23.	V_{CC} filter	18

1 Test conditions and connections of demonstration board

1.1 Power supply signal and interface connection

1. Connect the power supply to the +V_{CC} and GND terminal blocks (J2)
2. Connect the STEVAL-CCA053V1 interface board to the J4 connector
3. Connect the S/PDIF signal cable to the RCA jack on the STEVAL-CCA035V1 board. The signal source should be the Audio Precision equipment or a DVD player.
4. Adjust the voltage level of the power supply. The voltage range of the DC power supply is 4.5 V to 18 V.
5. Connect the load to the connectors J1 and J3

1.2 Output configuration


The STA333IS demonstration board can be only configured for 2.0 channels and BTL outputs.

1.3 Required equipment

- Audio Precision (System 2700)
 - Audio Analyzer: Mod. SYS2722 -192K
 - Class-D filter: AUX-0025 filter
 - Multifunction module: DCX-127
- DC power supply (4.5 V to 18 V)
 - Lambda Genesys Gen 80-19
 - HP 6038A
- Digital oscilloscope: Tektronix TDS5054B
- Digital multimeter: AGILENT Mod. 34410A
- PC with APWorkbench control software installed

1.4 Board connections

Figure 2. Demonstration board (four-layer) - connectors

 

2 Schematic diagram and PCB layout

2.1 Schematic

Figure 3. Schematic diagram - part 1



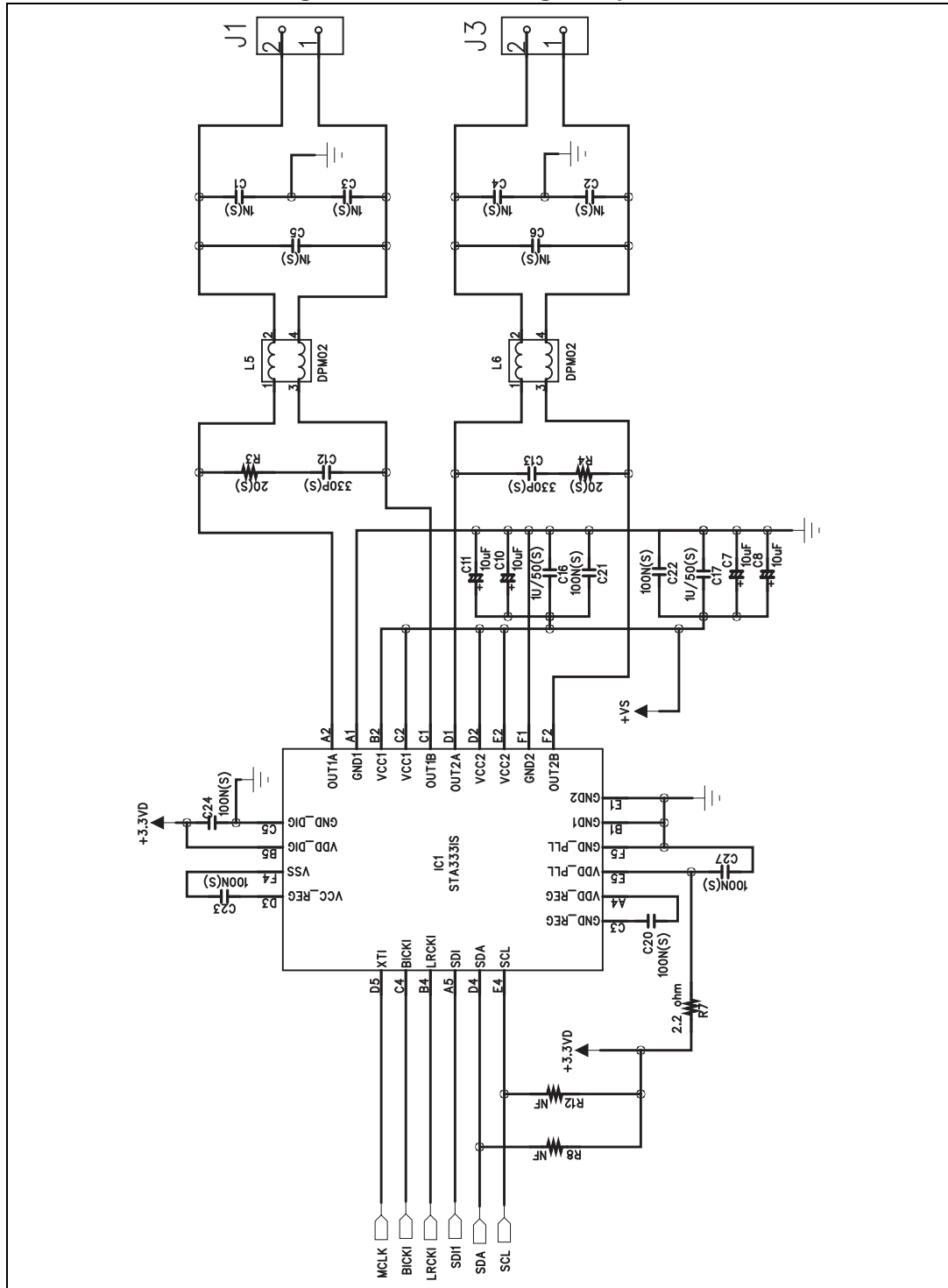


Figure 4. Schematic diagram - part 2 (connectors)

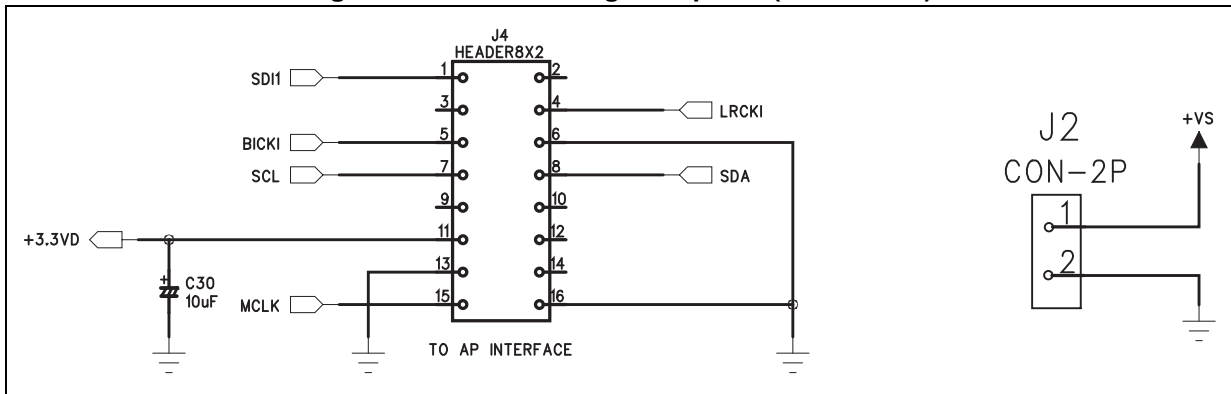

2.2 PCB layout

Figure 5. STEVAL-CCA053V1 board - four-layer PCB

 

Note: Please refer to [Figure 18](#) through [Figure 21](#) on page 17 for the top, inner layer 2, inner layer 3, and bottom views, respectively.

2.3 Bill of material

Table 1. Bill of material

No.	Type	Footprint	Description	Qty	Reference	Manufacturer
1	Connector	Through-hole	2P pitch: 5 mm connector terminal	3	J1, J2, J3	Any source
2	Header	Through-hole	16P (8 x 2 row) 2.5 mm header	1	J4	Any source
3	CCAP	CAP0603	50 Volt NPO 330 pF $\pm 10\%$	2	C12, C13	Murata
4	CCAP	CAP0603	50 Volt 1nF $\pm 10\%$	6	C1, C2, C3, C4, C5, C6	Murata
5	CCAP	CAP0603	50 Volt 100 nF $\pm 10\%$	6	C20, C21, C22, C23, C24, C27	Murata
6	CCAP	CAP1206	50 Volt 1U $\pm 10\%$	2	C16, C17	Murata
7	ECAP	CAP1206	10 μ F / 16 V	5	C7, C8, C10, C11, C30	Samsung
8	RES	R1206	6R2, $\pm 5\%$ 1/8W	4	R1, R2, R5, R6	Murata
9	RES	R1206	20 $\pm 5\%$ 1/8W	2	R3, R4	Murata
10	RES	R0603	2R2 $\pm 5\%$ 1/16W	1	R7	Murata
11	RES	R0603	NS	2	R8, R12	
12	Plastic rod		Hexagonal rod 15 mm length, male type	4	Four corners	Any source
13	Plastic rod		Hexagonal rod 8 mm length, female type	4	Four corners	Any source
14	IC	CSP 5x6 array	STA333IS	1	IC1	STMicroelectronics
15	Coil	SMD	DPM02, MARUWA	2	L5, L6	Maruwa
16	PCB		STA333IS 4-layer 1V0	1		Fastprint

3 APWorkbench settings

Figure 6. APWorkbench - device selection


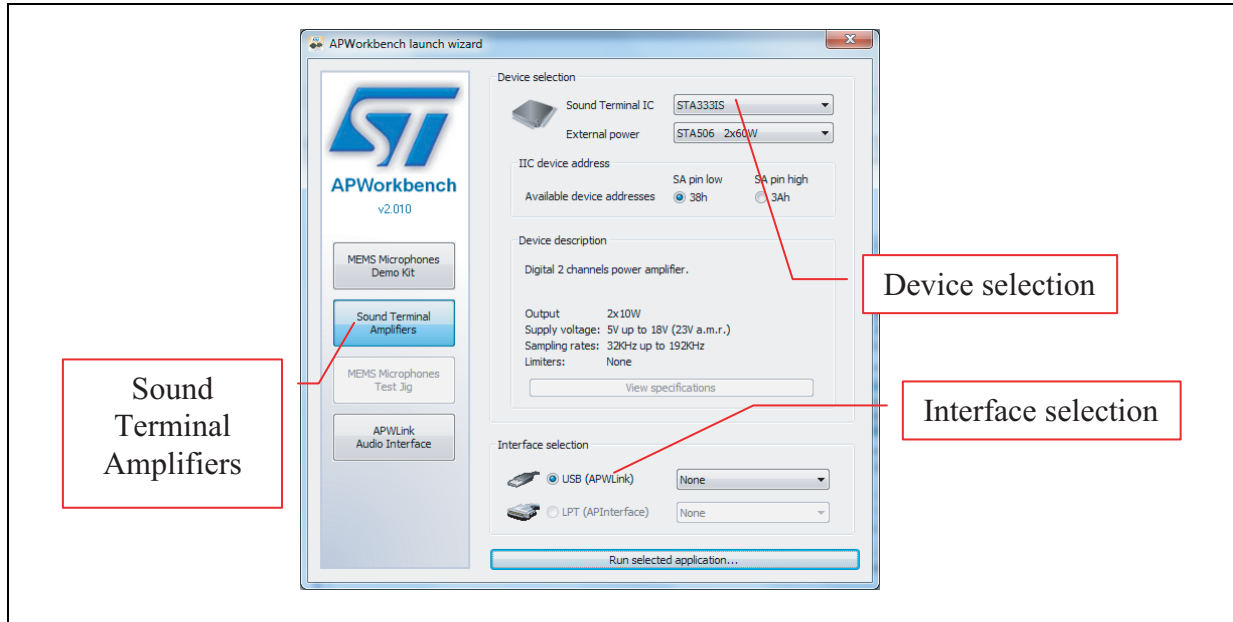


Figure 7. APWorkbench - control panel

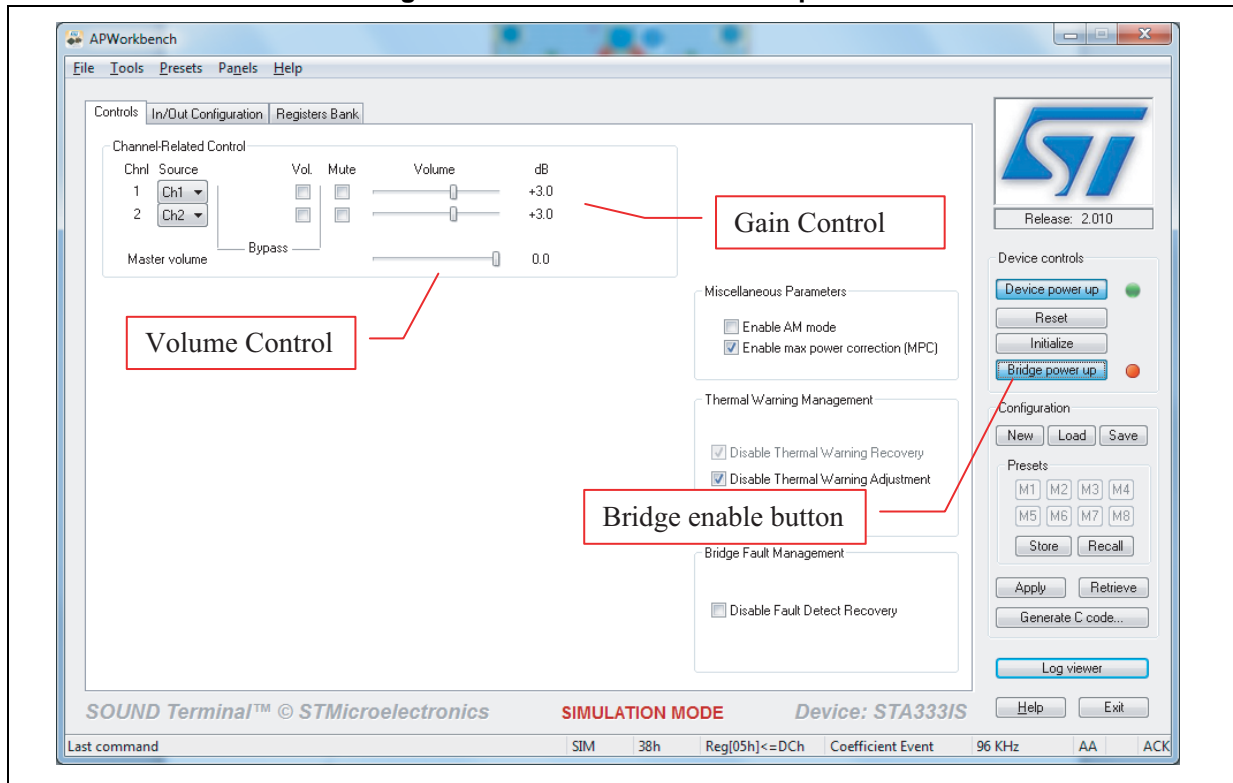

4 Test results

Figure 8. THD+N vs. power - $V_{CC} = 12.5\text{ V}$, load = $8\ \Omega$, 1 kHz

 


Figure 9. THD+N vs. frequency - $V_{CC} = 12.5\text{ V}$, load = $8\ \Omega$, Pout = 1 W at 1 kHz

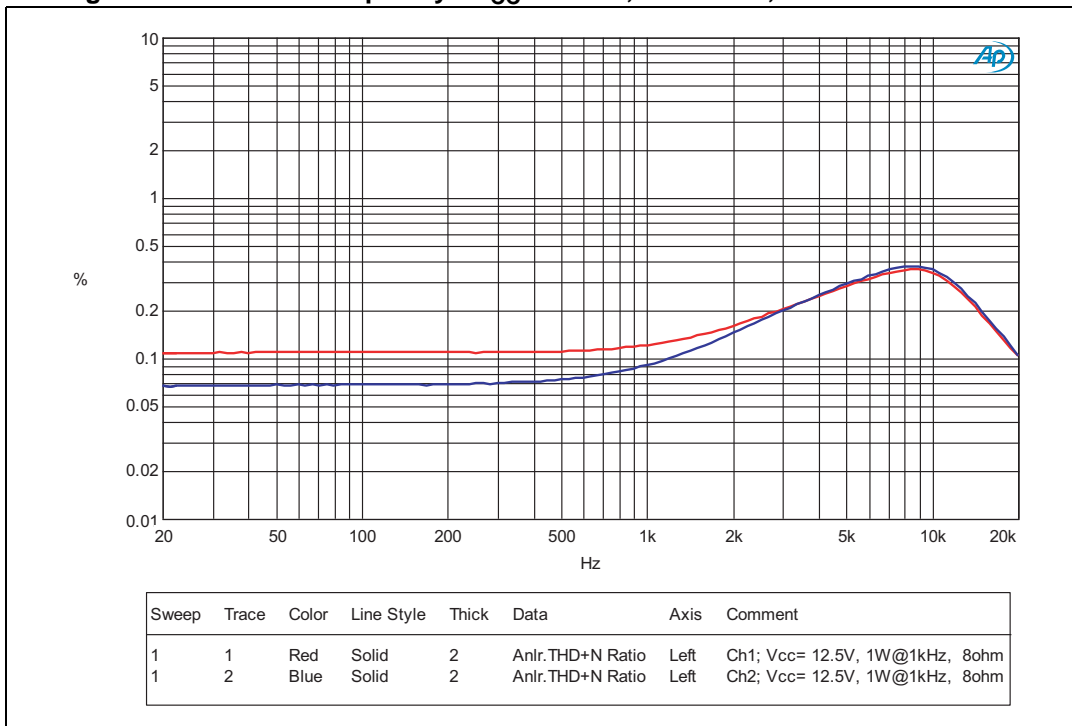


Figure 10. Frequency response - $V_{CC} = 12.5\text{ V}$, load = $8\ \Omega$, Pout = 1 W at 1 kHz

 


Figure 11. Crosstalk - $V_{CC} = 12.5\text{ V}$, load = $8\ \Omega$, Pout = 1 W at 1 kHz

 


Figure 12. FFT - $V_{CC} = 12.5\text{ V}$, load = $8\ \Omega$, $P_{out} = 1\text{ W}$ at 1 kHz

 


Figure 13. Output power vs. supply voltage - load = $8\ \Omega$, 1 kHz


 


Figure 14. Efficiency - $V_{CC} = 12.5\text{ V}$, 1 kHz , load = $8\ \Omega$ (stereo)

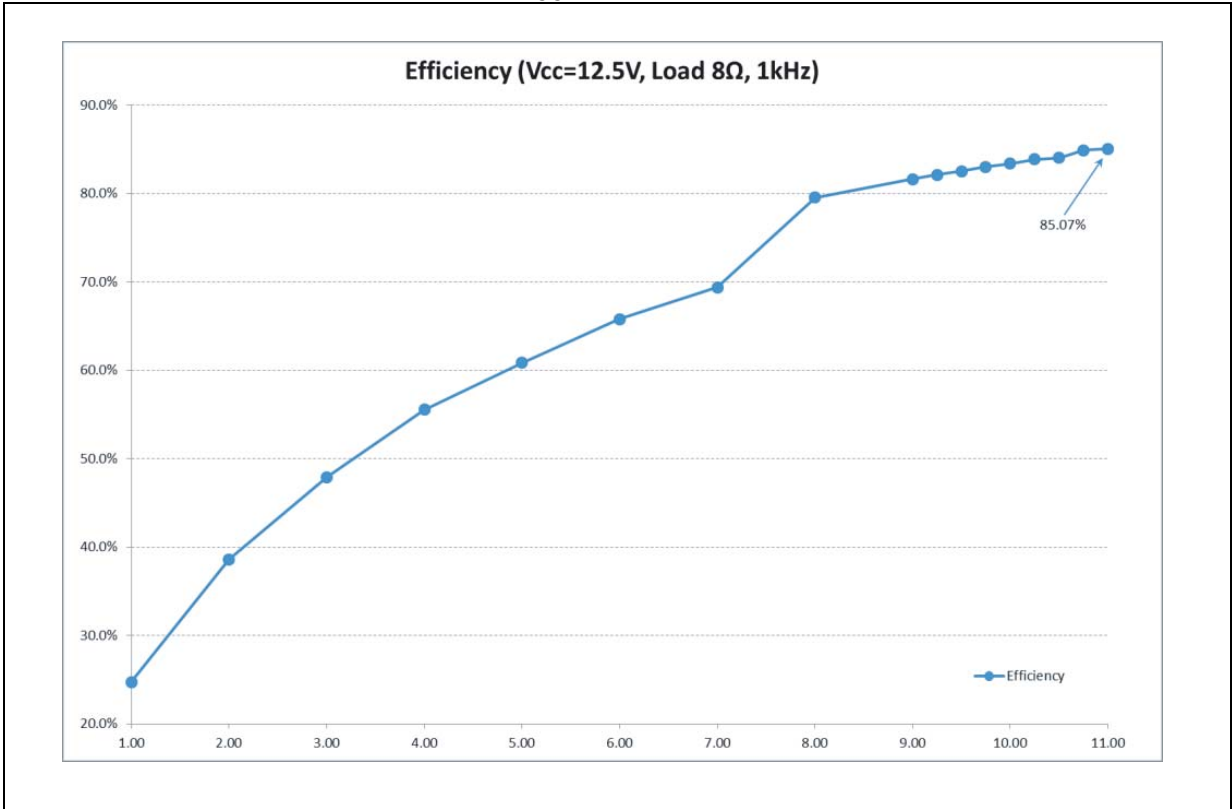

5 Thermal test - $V_{CC} = 12.5\text{ V}$, 1 kHz, load= 8 Ω (stereo)

5.1 Test conditions

$V_{CC} = 12.5\text{ VDC}$

Load= 8 Ω (resistive dummy load)

Gain= +3 dB (both L&R channels)

All channels ON

AP filter= 22 Hz ÷ 22 kHz

Output power: 2 x 10 W (adj. using post-scale)

$T_{amb} = 31\text{ }^{\circ}\text{C}$


5.2 Test results

$T_{max} = 88.6\text{ }^{\circ}\text{C}$

$T_{amb} = 31\text{ }^{\circ}\text{C}$

$\Delta T = 57.6\text{ }^{\circ}\text{C}$

Figure 15. Thermal analysis - $V_{CC} = 12.5\text{ V}$ - 2 x 10 W at 1 kHz

 

6 Design guidelines for schematic and PCB layout

6.1 General

- Absolute maximum rating: 20 V
- Bypass capacitor 100 nF in parallel to 1 μ F and 10 μ F for each power V_{CC} branch. Preferable dielectric is X7R.
- Vdd and ground for the digital section should be separated from the other power supply.
- Coil saturation current compatible with the peak current of the application

6.2 Decoupling capacitors

The decoupling capacitors can be shared for each V_{CC} branch. The decoupling capacitors must be placed as close as possible to the IC pins.

The capacitor and the decoupling capacitor must be on the same layer as well as the track used to connect the capacitors and the positive V_{CC} device pins.

6.3 Snubber network

The snubber circuit must be optimized for the specific application. Starting values are 330 pF in series to 22 Ω .

The power dissipation in this network can be defined by the following formula which considers the power supply, frequency and capacitor value:

$$P = C \cdot \text{Freq}_{\text{PWM}} \cdot (2 \cdot V_{\text{OUT}})^2$$


This power is dissipated on the series resistance.

6.4 PCB layout

6.4.1 Snubber layout

Solder the snubber network as close as possible to the related IC pin.


Figure 16. Snubber network

 

6.4.2 V_{CC} traces

Design the PCB tracks to implement a star routing for the V_{CC} traces.

Figure 17. PCB layout recommendations - star routing V_{CC} traces

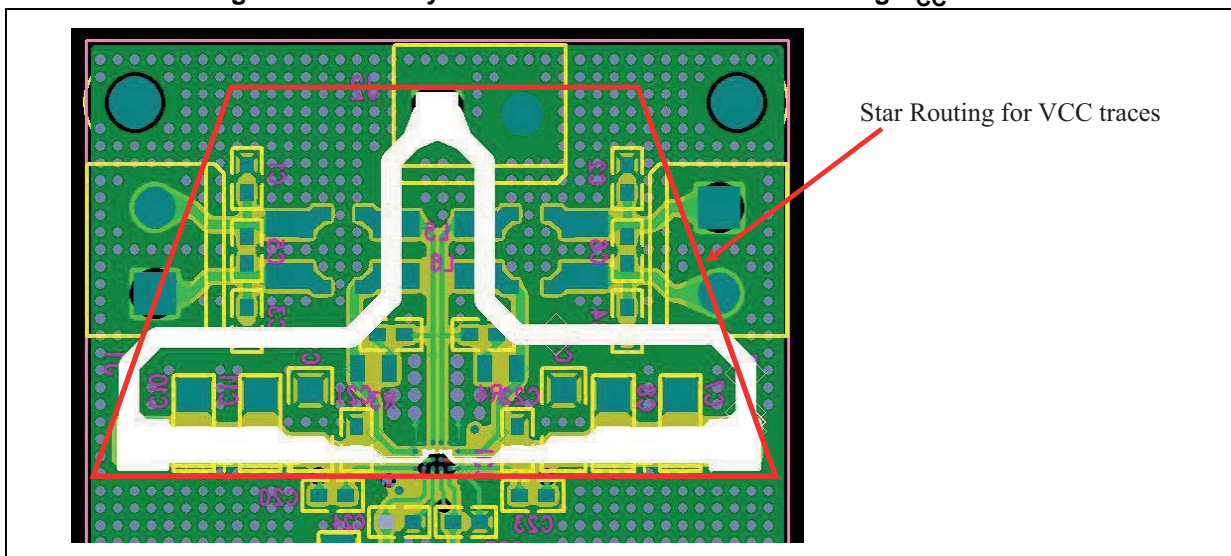

6.4.3 Ground plane and heatsink

To dissipate the power not delivered to the loads, a large ground plane should be implemented. This solution allows removing the heat from the device without adding an external heatsink.

Note: It is mandatory to have a large ground plane on the top layer, inner layer 2, inner layer 3, and the bottom layer and solder the slug on the PCB.

Figure 18. PCB layout recommendation - large ground plane on the top side

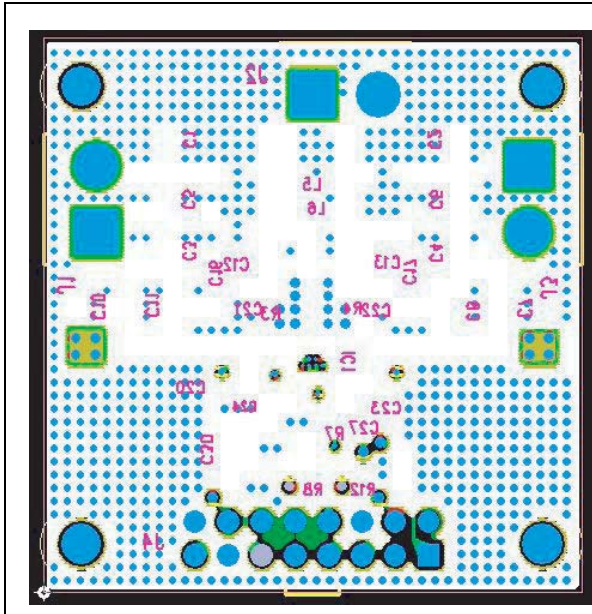


Figure 19. PCB layout recommendation - large ground plane on the inner layer 2

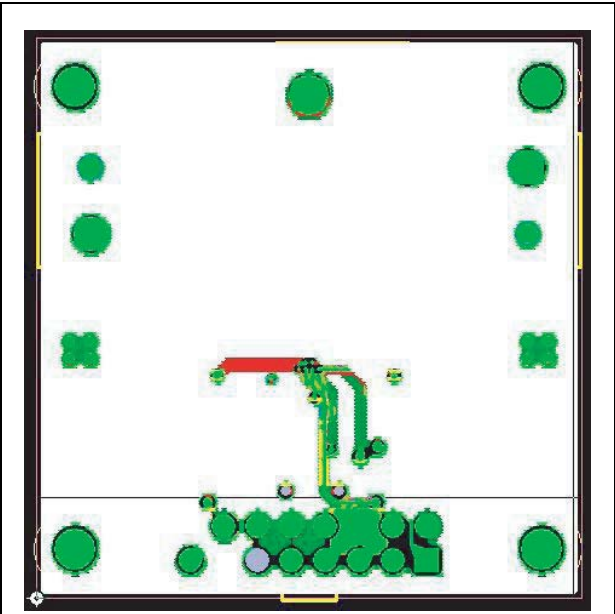


Figure 20. PCB layout recommendation - large ground plane on the inner layer 3


 



Figure 21. PCB layout recommendation - large ground plane on the bottom side

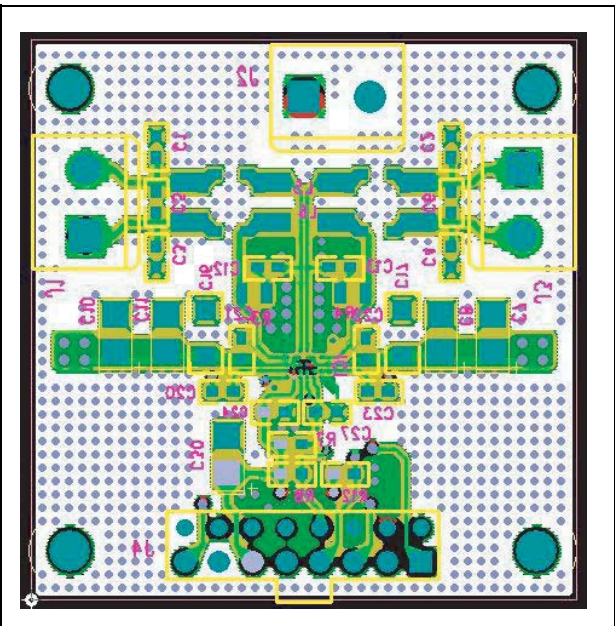

6.4.4 Output filter

It is recommended to design the PCB using symmetrical paths and tracks.


Figure 22. Output filter

 

6.4.5 V_{CC} filter for high frequency

The V_{CC} filter capacitors must be placed as close as possible to the supply pins. The ceramic capacitors must be positioned on the same layer of the device (in this demonstration board, on the top layer of the PCB) and the distance from the IC must be short and compatible with the minimum SMB mounting limitation.

Figure 23. V_{CC} filter

 

The PWM frequency is 384 kHz (with F_s = 48 kHz) with very fast transition time. In order to compensate the inductive effect of the copper track, the ceramic capacitors must be placed as close as possible to the supply pins. The recommended distance between the capacitors and the supply pins is less than 5 mm.

7 Revision history

Table 2. Document revision history

Date	Revision	Changes
01-Jul-2013	1	Initial release.

Please Read Carefully:

Information in this document is provided solely in connection with ST products. STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, modifications or improvements, to this document, and the products and services described herein at any time, without notice.

All ST products are sold pursuant to ST's terms and conditions of sale.

Purchasers are solely responsible for the choice, selection and use of the ST products and services described herein, and ST assumes no liability whatsoever relating to the choice, selection or use of the ST products and services described herein.

No license, express or implied, by estoppel or otherwise, to any intellectual property rights is granted under this document. If any part of this document refers to any third party products or services it shall not be deemed a license grant by ST for the use of such third party products or services, or any intellectual property contained therein or considered as a warranty covering the use in any manner whatsoever of such third party products or services or any intellectual property contained therein.

UNLESS OTHERWISE SET FORTH IN ST'S TERMS AND CONDITIONS OF SALE ST DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY WITH RESPECT TO THE USE AND/OR SALE OF ST PRODUCTS INCLUDING WITHOUT LIMITATION IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE (AND THEIR EQUIVALENTS UNDER THE LAWS OF ANY JURISDICTION), OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

ST PRODUCTS ARE NOT AUTHORIZED FOR USE IN WEAPONS. NOR ARE ST PRODUCTS DESIGNED OR AUTHORIZED FOR USE IN: (A) SAFETY CRITICAL APPLICATIONS SUCH AS LIFE SUPPORTING, ACTIVE IMPLANTED DEVICES OR SYSTEMS WITH PRODUCT FUNCTIONAL SAFETY REQUIREMENTS; (B) AERONAUTIC APPLICATIONS; (C) AUTOMOTIVE APPLICATIONS OR ENVIRONMENTS, AND/OR (D) AEROSPACE APPLICATIONS OR ENVIRONMENTS. WHERE ST PRODUCTS ARE NOT DESIGNED FOR SUCH USE, THE PURCHASER SHALL USE PRODUCTS AT PURCHASER'S SOLE RISK, EVEN IF ST HAS BEEN INFORMED IN WRITING OF SUCH USAGE, UNLESS A PRODUCT IS EXPRESSLY DESIGNATED BY ST AS BEING INTENDED FOR "AUTOMOTIVE, AUTOMOTIVE SAFETY OR MEDICAL" INDUSTRY DOMAINS ACCORDING TO ST PRODUCT DESIGN SPECIFICATIONS. PRODUCTS FORMALLY ESCC, QML OR JAN QUALIFIED ARE DEEMED SUITABLE FOR USE IN AEROSPACE BY THE CORRESPONDING GOVERNMENTAL AGENCY.

Resale of ST products with provisions different from the statements and/or technical features set forth in this document shall immediately void any warranty granted by ST for the ST product or service described herein and shall not create or extend in any manner whatsoever, any liability of ST.

ST and the ST logo are trademarks or registered trademarks of ST in various countries.

Information in this document supersedes and replaces all information previously supplied.

The ST logo is a registered trademark of STMicroelectronics. All other names are the property of their respective owners.

© 2013 STMicroelectronics - All rights reserved

STMicroelectronics group of companies

Australia - Belgium - Brazil - Canada - China - Czech Republic - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan - Malaysia - Malta - Morocco - Philippines - Singapore - Spain - Sweden - Switzerland - United Kingdom - United States of America

www.st.com