

SANYO Semiconductors

DATA SHEET

An ON Semiconductor Company

N-Channel Silicon MOSFET BMS4007 — General-Purpose Switching Device **Applications**

Features

- ON-resistance $R_{DS}(on)=6m\Omega$ (typ.)
- Input capacitance Ciss=9700pF (typ.)
- 10V drive

Specifications


Absolute Maximum Ratings at Ta=25°C

Parameter	Symbol	Conditions	Ratings	Unit
Drain-to-Source Voltage	VDSS		75	V
Gate-to-Source Voltage	VGSS		±20	V
Drain Current (DC)	ID		60	А
Drain Current (Pulse)	IDP	PW≤10μs, duty cycle≤1%	240	А
Allowable Power Dissipation	PD		2.0	W
		Tc=25°C	30	W
Channel Temperature	Tch		150	°C
Storage Temperature	Tstg		-55 to +150	°C
Avalanche Energy (Single Pulse) *1	EAS		299	mJ
Avalanche Current *2	IAV		48	А

Note :*1 VDD=48V, L=100µH, IAV=48A (Fig.1) *2 L≤100µH, Single pulse

Package Dimensions



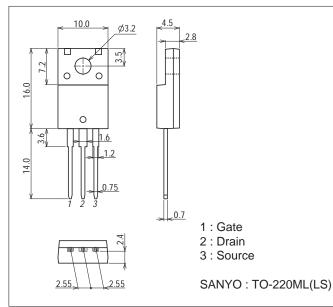


Product & Package Information

- Package : TO-220ML(LS)
- JEITA, JEDEC : SC-67, SOT-186A
- Minimum Packing Quantity: 100 pcs./bag or 50pcs./magazine

Marking

Electrical Connection



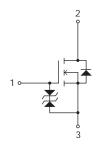

SANYO Semiconductor Co., Ltd. http://semicon.sanyo.com/en/network

Electrical Characteristics at Ta=25°C

Parameter	Symbol	Conditions		Ratings		
			min	typ	max	Unit
Drain-to-Source Breakdown Voltage	V(BR)DSS	ID=1mA, VGS=0V	75			V
Zero-Gate Voltage Drain Current	IDSS	V _{DS} =75V, V _{GS} =0V			10	μΑ
Gate-to-Source Leakage Current	IGSS	V _{GS} =±16V, V _{DS} =0V			±10	μΑ
Cutoff Voltage	VGS(off)	V _{DS} =10V, I _D =1mA	2		4	V
Forward Transfer Admittance	yfs	VDS=10V, ID=30A		110		S
Static Drain-to-Source On-State Resistance	R _{DS} (on)	ID=30A, VGS=10V		6	7.8	mΩ
Input Capacitance	Ciss	V _{DS} =20V, f=1MHz		9700		рF
Output Capacitance	Coss			540		рF
Reverse Transfer Capacitance	Crss			360		pF
Turn-ON Delay Time	t _d (on)	- See Fig.2		100		ns
Rise Time	tr			180		ns
Turn-OFF Delay Time	t _d (off)			460		ns
Fall Time	tf			160		ns
Total Gate Charge	Qg	V _{DS} =48V, V _{GS} =10V, I _D =60A		160		nC
Gate-to-Source Charge	Qgs			40		nC
Gate-to-Drain "Miller" Charge	Qgd			40		nC
Diode Forward Voltage	V _{SD}	IS=60A, VGS=0V		0.9	1.2	V
Reverse Recovery Time	trr	See Fig.3		70		ns
Reverse Recovery Charge	Q _{rr}	IS=60A, VGS=0V, di/dt=100A/μs		183		nC

Fig.1 Avalanche Resistance Test Circuit

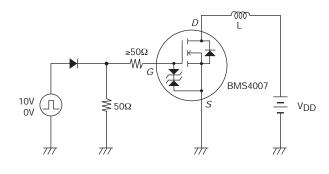


Fig.2 Switching Time Test Circuit





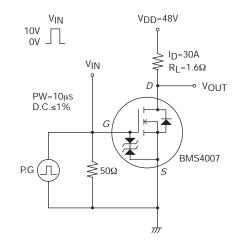


Fig.3 Reverse Recovery Time Test Circuit

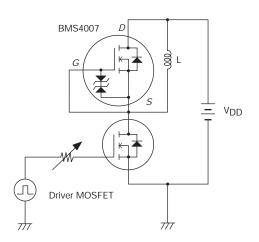

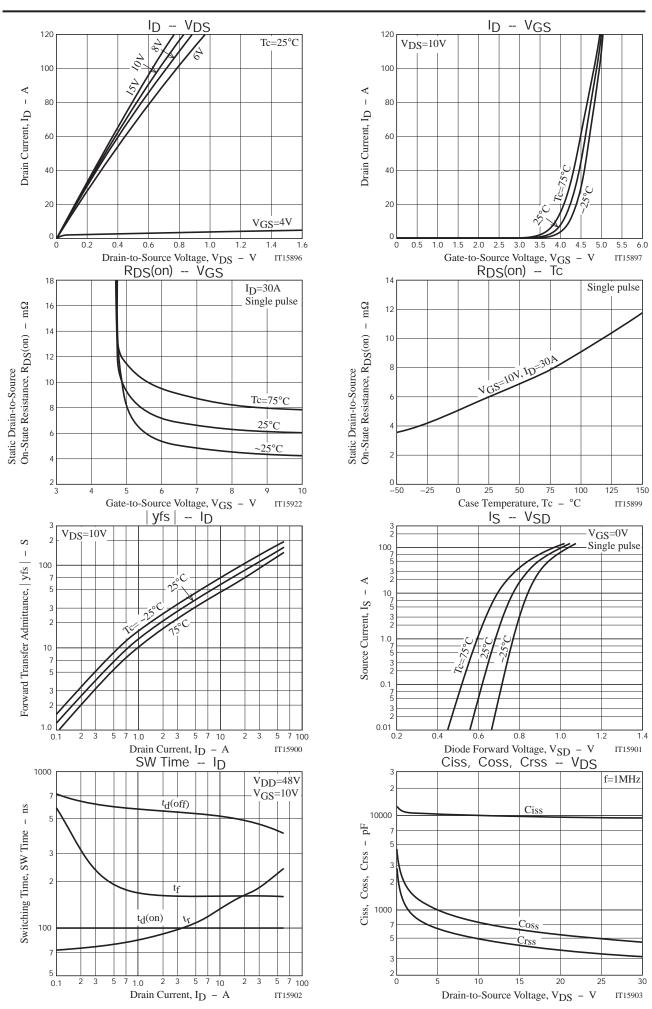

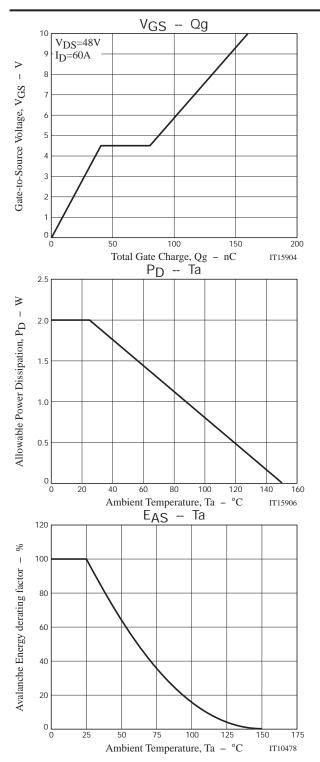

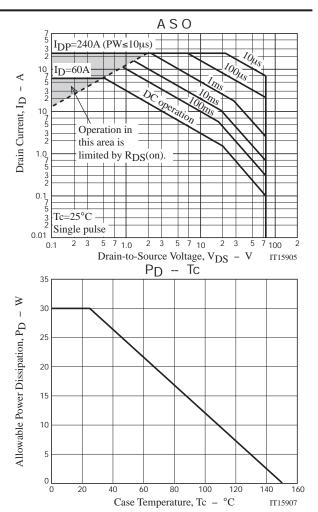

Note on usage : Since the BMS4007 is a MOSFET product, please avoid using this device in the vicinity of highly charged objects.

- Any and all SANYO Semiconductor Co.,Ltd. products described or contained herein are, with regard to "standard application", intended for the use as general electronics equipment (home appliances, AV equipment, communication device, office equipment, industrial equipment etc.). The products mentioned herein shall not be intended for use for any "special application" (medical equipment whose purpose is to sustain life, aerospace instrument, nuclear control device, burning appliances, transportation machine, traffic signal system, safety equipment etc.) that shall require extremely high level of reliability and can directly threaten human lives in case of failure or malfunction of the product or may cause harm to human bodies, nor shall they grant any guarantee thereof. If you should intend to use our products for applications outside the standard applications, please consult with us prior to the intended use. If there is no consultation or inquiry before the intended use, our customer shall be solely responsible for the use.
- Specifications of any and all SANYO Semiconductor Co.,Ltd. products described or contained herein stipulate the performance, characteristics, and functions of the described products in the independent state, and are not guarantees of the performance, characteristics, and functions of the described products as mounted in the customer's products or equipment. To verify symptoms and states that cannot be evaluated in an independent device, the customer should always evaluate and test devices mounted in the customer's products or equipment.
- SANYO Semiconductor Co.,Ltd. assumes no responsibility for equipment failures that result from using products at values that exceed, even momentarily, rated values (such as maximum ratings, operating condition ranges, or other parameters) listed in products specifications of any and all SANYO Semiconductor Co.,Ltd. products described or contained herein.
- SANYO Semiconductor Co.,Ltd. strives to supply high-quality high-reliability products, however, any and all semiconductor products fail or malfunction with some probability. It is possible that these probabilistic failures or malfunction could give rise to accidents or events that could endanger human lives, trouble that could give rise to smoke or fire, or accidents that could cause damage to other property. When designing equipment, adopt safety measures so that these kinds of accidents or events cannot occur. Such measures include but are not limited to protective circuits and error prevention circuits for safe design, redundant design, and structural design.
- In the event that any or all SANYO Semiconductor Co.,Ltd. products described or contained herein are controlled under any of applicable local export control laws and regulations, such products may require the export license from the authorities concerned in accordance with the above law.
- No part of this publication may be reproduced or transmitted in any form or by any means, electronic or mechanical, including photocopying and recording, or any information storage or retrieval system, or otherwise, without the prior written consent of SANYO Semiconductor Co.,Ltd.
- Any and all information described or contained herein are subject to change without notice due to product/technology improvement, etc. When designing equipment, refer to the "Delivery Specification" for the SANYO Semiconductor Co.,Ltd. product that you intend to use.
- Information (including circuit diagrams and circuit parameters) herein is for example only; it is not guaranteed for volume production.
- Upon using the technical information or products described herein, neither warranty nor license shall be granted with regard to intellectual property rights or any other rights of SANYO Semiconductor Co.,Ltd. or any third party. SANYO Semiconductor Co.,Ltd. shall not be liable for any claim or suits with regard to a third party's intellectual property rights which has resulted from the use of the technical information and products mentioned above.

This catalog provides information as of August, 2010. Specifications and information herein are subject to change without notice.