IGBT Gate Driver

DESCRIPTION

RT8H255C is a integrating IGBT gate drive circuit.

This product can drive IGBT with two external transistors. GATEIN terminal have hysteresis input voltage.


Case of "L→H" propagation, B terminal output low signal at over 2.80V. Case of "H→L" propagation, B terminal output high signal at under 2.48V.


FEATURE

The miniaturization of a set and high-density mounting are possible.

APPLICATION

IGBT Gate Driver

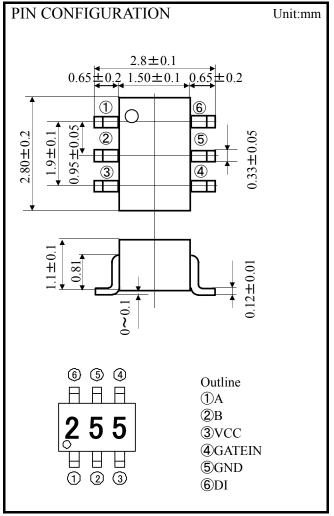

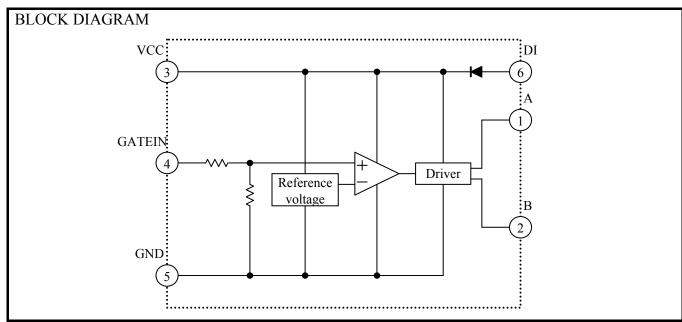

IGBT Gate Driver


ABSOLUTE MAXIMUM RATINGS (Ta=25°C, unless otherwise noted)

Symbol	Parameter	Conditions	Ratings	Unit
Vcc	Supply voltage		30	V
VGIN	IN terminal voltage		10	V
Pd	Power Dissipation	Ta≧25°C	200	mW
Кθ	Thermal derating factor		1.6	mW/°C
Tj	Junction temperature		150	°C
Tstg	Storage temperature	Non condensing	−40~150	°C
Topr	Operating temperature	Non condensing	−20~75	°C


ELECTRICAL CHARACTERISTICS (Ta=25°C, VCC=20V, Terminal is open, unless otherwise notec)


Symbol	Parameter	Test conditions		Limits		
			Min.	Typ.	Max.	Unit
Vcc	Operating supply voltage range		10	20	25	V
ICC1	Circuit current 1	GATEIN=0V	-	490	735	uA
ICC2	Circuit current 2	GATEIN=5V	-	500	750	uA
VOB2	B terminal output low voltage 2	GATEIN=5V	-	0	0.28	V
Vth1	GATEIN terminal threshold voltage 1 (Low→High)	GATEIN:0→5V VMB:Low	2.54	2.80	3.10	V
Vth2	GATEIN terminal threshold voltage 2(High→Low)	GATEIN:5→0V VMB:High	2.24	2.48	2.74	V
IOUTA1	A terminal output current 1	GATEIN=0V, A=B=0.7V IMA	-1	0	1	uA
IOUTA2	A terminal output current 2	GATEIN=5V, A=18V IMA	-810	-600	-390	uA
IINB	B terminal sink current	GATEIN=5V, B=0.3V IMB	700	1080	1460	uA
IOUTB	B terminal source current	GATEIN=0V, B=0.7V IMB	-1120	-830	-540	uA


IGBT Gate Driver

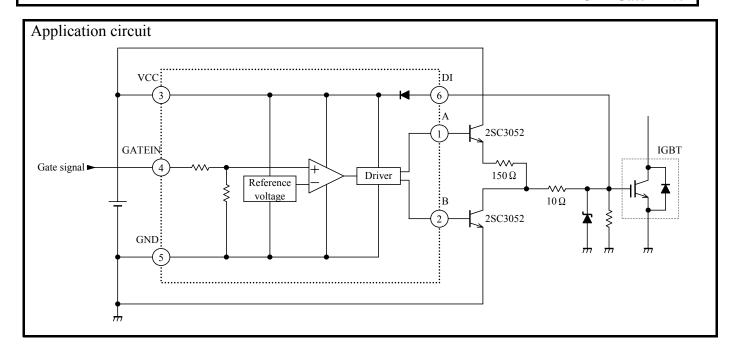


<TYPICAL CHARACTERISTICS>

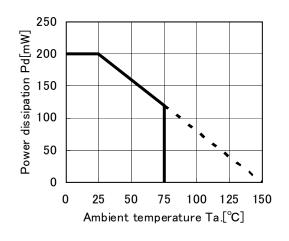


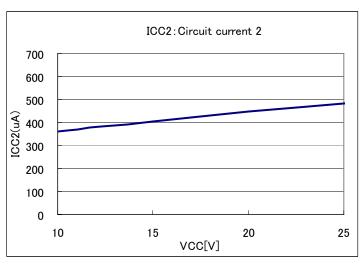


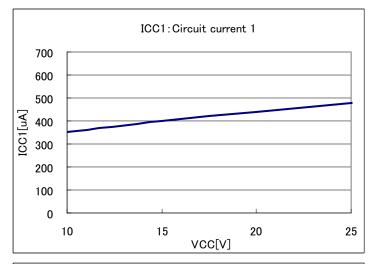


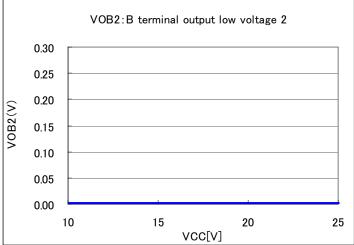



IGBT Gate Driver

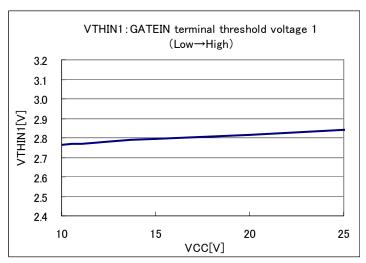


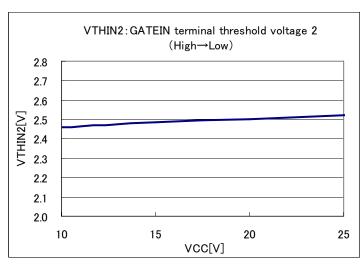

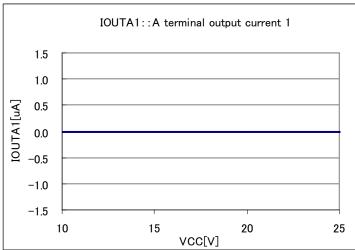

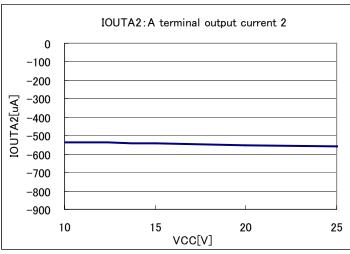

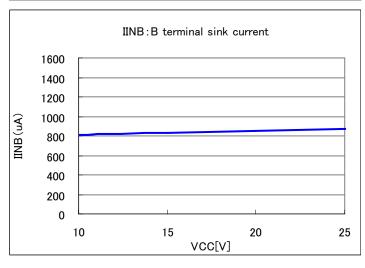

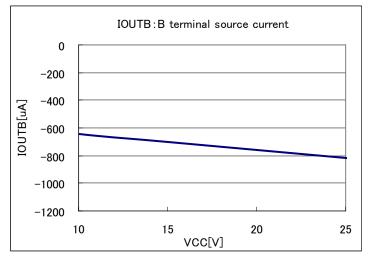



Marketing division, Marketing planning department 6-41 Tsukuba, Isahaya, Nagasaki, 854-0065 Japan

Keep safety first in your circuit designs!

ISAHAYA Electronics Corporation puts the maximum effort into making semiconductor products better and more reliable, but there is always the possibility that trouble may occur with them. Trouble with semiconductors may lead to personal injury, fire or property damage. Remember to give due consideration to safety when making your circuit designs, with appropriate measures such as (1) placement of substitutive, auxiliary, (2) use of non-farmable material or (3) prevention against any malfunction or mishap.

Notes regarding these materials

- These materials are intended as a reference to our customers in the selection of the ISAHAYA products best suited to the customer's application; they don't convey any license under any intellectual property rights, or any other rights, belonging
- Customer's application; they don't convey any license under any intellectual property rights, or any other rights, belonging ISAHAYA or third party.

 ISAHAYA or third party.

 ISAHAYA Electronics Corporation assumes no responsibility for any damage, or infringement of any third party's rights, originating in the use of any product data, diagrams, charts or circuit application examples contained in these materials.

 All information contained in these materials, including product data, diagrams and charts, represent information on products at the time of publication of these materials, and are subject to change by ISAHAYA Electronics Corporation without notice due to product improvements or other reasons. It is therefore recommended that customers contact ISAHAYA Electronics Corporation or an authorized ISAHAYA products distributor for the latest product information before purchasing product listed
- ISAHAYA Electronics Corporation products are not designed or manufactured for use in a device or system that is used under circumstances in which human life is potentially at stake. Please contact ISAHAYA electronics corporation or an authorized ISAHAYA products distributor when considering the use of a product contained herein for any specific purposes, such as apparatus or systems for transportation, vehicular, medical, aerospace, nuclear, or undersea repeater use.

 The prior written approval of ISAHAYA Electronics Corporation is necessary to reprint or reproduce in whole or in part these
- If these products or technologies are subject to the Japanese export control restrictions, they must be exported under a license from the Japanese government and cannot be imported into a country other than the approved destination. Any diversion or re-export contrary to the export control laws and regulations of Japan and/or the country of destination is prohibited.

 •Please contact ISAHAYA Electronics Corporation or authorized ISAHAYA products distributor for further details on these
- materials or the products contained therein.